

CONTENT.

Serial No

Content.

Page No

1

MOS DEVICE PHYSICS

1

2

SINGLE STAGE AMPLIFIER

12

3

MOS DEVICE PHYSICS.

→ The level of abstraction of knowledge required to study analog is

Quantum physics → Solid state physics → Semiconductor physics
→ device Modelling → design of circuits.


Mosfet as switch.

* To use mosfet as a switch. the drain to source Resistance should be very low. when gate voltage of mosfet (nmos) is very high, in ideal case it should be zero. & the resistance should be very high for low gate voltage. in ideal case it should be infinity.

Mosfet structure.

* The effective length of mosfet is given by $L_{\text{drawn}} - 2L_D = L_{\text{eff}}$


 
* mosfet is a symmetrical device i.e the drain & source of the device can be interchanged.



* The substrate of the mosfet must be reverse bias with respect to source. or else the current will directly flow from S/D to the substrate. if it is forward bias. this is called latch up.


* Pmos is negation of nmos. & it is fabricated in an N-well & substrate. is connected to highest potential.

Mosfet Symbol

  

Mosfet V-I characteristics.

* When we apply voltage to the gate, the holes move away from gate and electron move towards the gate. this will create a channel. if we increase V_g then the depletion region will increase. this region can be modelled as two cap i.e gate oxide cap & depletion cap connected in series. if we increase V_g the current will start to flow. then we can say device is inverted. the V_g required for this inverted channel is called V_{TH} . if V_g is increased further the charge in depletion region will be same but charge density i.e current will increase.

 

$$V_{TH} = \phi_{ms} + 2\phi_f + \frac{\phi_{dep}}{C_{ox}}$$

ϕ_{ms} :- Polysilicon & silicon workfunction.

$$\phi_f = V_T \ln\left(\frac{N_{sub}}{N_i}\right)$$

$N_{sub} \rightarrow$ charge density. $N_i \rightarrow$ intrinsic carrier
 $V_T =$ thermal voltage.

$$\phi_{dep} = \sqrt{4q\epsilon_{si}|\phi_f|N_{sub}}$$

$$C_{ox} = \frac{\epsilon_{si}}{t_{ox}} \approx 17.25 \text{ fF}/\mu\text{m}^2$$

* for Pmos theory is same but the polarity is reversed.

Derivation of I-V characteristics.

* Current is the amount of charge flowed per unit time i.e. it is equal to

$$I_D = Q_d \cdot V \quad (1)$$

$Q_d \rightarrow$ charge density
 $V \rightarrow$ velocity of charge.



* for $V_{GS} > V_{th}$ the charge density is proportional to $V_{GS} - V_{th}$. For $V_{GS} \leq V_{th}$, $Q_d = 0$.

$$Q_d = W C_{ox} (V_{GS} - V_{th}) \quad (2)$$

* When we increase $V_{DS} > 0$ the channel potential varies from $V_G(x) = 0$ to $V_D(x) = V_{DD}$. \therefore the charge density can be written as.

$$Q_d = W C_{ox} (V_{GS} - V_{th} - V(x)) \quad (3) \quad V(x) \text{ varies from } 0 \text{ to } V_D.$$

* Substitute equation 3 into 1.

$$I_D = -W C_{ox} (V_{GS} - V_{th} - V(x)) \cdot V \quad (4) \quad V \rightarrow \text{velocity of electron.}$$

* Negative sign is due to negative charge we know that.

$$V = \mu_n \vec{E} \Rightarrow V = \mu_n \left(-\frac{dV}{dx} \right) \quad (5) \quad V \Rightarrow \text{potential.}$$

Substituting equation 5 in 4.

$$I_D = W C_{ox} (V_{GS} - V_{th} - V(x)) \times \mu_n \times \frac{dV}{dx}$$

Integrating on both side.

$$\int_0^L I_{D0} dx = \int_{V_{DS}=0}^{V_{DS}=V_{DD}} W C_{ox} (V_{GS} - V_{th} - V(x)) \times \mu_n \times dV$$

\therefore the current in channel is given by

$$I_D = \frac{W C_{ox} \mu_n}{L} \left[(V_{GS} - V_{th}) V_{DS} - \frac{V_{DS}^2}{2} \right]$$

* for $V_{GS} - V_{th} \geq V_{DS}$ \therefore the device act as Voltage controlled resistor.

$$I_D \approx \frac{W C_{ox} \mu_n}{L} (V_{GS} - V_{th}) V_{DS}$$

$$\therefore R_{on} = \frac{1}{\frac{W}{L} C_{ox} \mu_n (V_{GS} - V_{th})}$$

* for $V_{GS} - V_{th} < V_{DS}$ the current in the mosfet become constant due to the pinch off. the effective length of transistor decrease. there is current even after the pinch off because there is large electric field in the channel. which will shoot electron to the drain of mosfet.

$$I_D = \frac{W C_{ox} \mu_n}{2 \times L'} (V_{GS} - V_{th})^2$$


* In saturation mosfet act as the current source when L is constant. Nmos current source inject current into ground. Where as pmos current source draw current from the V_{DD} .

MOS Transconductance.

→ The change in drain current with change in gate-source voltage is called transconductance. it is denoted by g_m .

$$g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{V_{DS} \text{ const}} \Rightarrow \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}).$$

 
$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})$$



$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D}$$



$$g_m = \frac{2 I_D}{V_{GS} - V_{TH}}$$

 

* g_m increases with overdrive voltage when W/L kept constant whereas g_m decrease with overdrive voltage when I_D is kept constant.

* the pinch off occurs when Voltage of drain is at $V_{GS} - V_{Th}$ if voltage of drain is increased further the effective length of mosfet is decreased and current is given by

$$I_D = \frac{\mu_n W}{L'} C_{ox} (V_{GS} - V_{Th})^2 \quad L' \rightarrow \text{effective length after pinch off}$$

* mobility of electron is twice the mobility of holes

> Transconductance of mosfet

$$* \quad g_m = \left. \frac{\partial I_D}{\partial V_{GS}} \right|_{\text{constant } V_{DS}} \Rightarrow \frac{\mu_n W}{L} C_{ox} (V_{GS} - V_{Th}) \Rightarrow \sqrt{\frac{\mu_n W}{L} C_{ox} I_D}$$

Body effect.

→ when Negative Voltage is applied to the body, more positive charge hole move towards the body which will increase the channel width. in order to balance this charge we need to add more positive charge to the gate. this will increase the V_{Th} of the transistor.

$$V_{Th} = V_{Th0} + \gamma \left[\sqrt{2\phi_f + \phi_{SB}} - \sqrt{2\phi_f} \right] \quad \gamma = \frac{\sqrt{2q\epsilon_s N_{sub}}}{C_{ox}}$$

→ γ range is from 0.3 to 0.4

channel length modulation.

→ The length of the channel will decrease when the voltage of the drain. increase. in other words the current i_d is function of V_{DS} . the effective change in length is given by.

$$L' = L - \Delta L. \quad \therefore \frac{L'}{L} = 1 - \frac{\Delta L}{L}$$

$$I_D = \frac{kW}{L \times \frac{L'}{L}} (V_{GS} - V_T)^2 \Rightarrow \frac{kW}{L \times \left[1 - \frac{\Delta L}{L}\right]} (V_{GS} - V_T)^2 \quad k \Rightarrow \frac{C_{ox} \mu_n}{2}$$

$$I_D \approx \frac{kW}{L} (V_{GS} - V_T)^2 \left[1 + \frac{\Delta L}{L}\right]$$


$$\frac{\Delta L}{L} \propto V_{DS} \Rightarrow \frac{\Delta L}{L} = \lambda V_{DS}$$

$$I_D \approx \frac{kW}{L} (V_{GS} - V_T)^2 [1 + \lambda V_{DS}]$$

→ λ is called channel modulation coefficient

→ the gm of the transistor is .
 
$$g_m = \frac{2kW}{L} (V_{GS} - V_T) [1 + \lambda V_{DS}]$$



→ This formula is less accurate for small channel mosfet. In short channel mosfet I_D is also dependent on V_{DS} .

Subthreshold conductance.

→ we have assumed that the current in mosfet is zero for $V_{GS} < V_T$ but this assumption is not right. there is current in the channel. this current is due to the weak inversion. & the current will rise exponentially with respect to V_{GS} . when subthreshold current reaches 100nA the gate voltage is taken as V_T of transistor.


$$I_D = I_0 e^{\frac{V_{GS} - V_T}{nV_T}} \quad I_0 \propto \frac{W}{L} \quad n \rightarrow \text{ideality factor} \quad V_T \rightarrow \text{thermal voltage.}$$

→ for voltage below V_T the current will drop 10 time per 80mV of voltage drop.

Mos device model :-

→ Parasitic caps of mosfet

 - gate to channel $\rightarrow C_1$ (oxide).
- channel to substrate $\rightarrow C_2$ (depletion)
- gate to source & drain $\rightarrow C_3 \& C_4 \rightarrow$ (overlap).
- Substrate to source & drain $\rightarrow C_5 \& C_6 \rightarrow$ (junction)



$$C_1 = WL C_{ox} \quad C_{ox} = \epsilon / t_{ox}$$


$$C_2 = WL \sqrt{q \epsilon_s N_{sub} / (4 \phi_F)}$$

$N_{sub} \rightarrow$ donor concentration.

$\phi_F \rightarrow$ voltage drop.

$$C_3 \& C_4 \Rightarrow C_{ox} L_0 \times W$$
 
$$\Rightarrow C_{ov} W \rightarrow C_{ov} \rightarrow \text{overlap cap per unit width.}$$



$C_5 \& C_6$

- $C_j \times \text{Area} \rightarrow$ due to bottom plate.
- $C_{jsw} \times \text{Perimeter} \rightarrow$ due to side wall (perimeter)

$$C_j = C_{j0} / \left[1 + \frac{V_R}{\phi_B} \right]^m$$

→ $V_R \rightarrow$ reverse bias voltage.
 → $\phi_B \rightarrow$ built in potential.
 $m \rightarrow 0.3 \text{ to } 0.4$

→ Similar for C_{jsw}

→ C_{jsw} for region marked in yellow from figure 1 may be different compared to region marked in pink. but we assume it is equal to other regions



P
Fig 1

Case I \Rightarrow when device is off $V_{GS} < V_{Th}$.

1) $C_{qD} = C_{qS} = C_{ov}W$


2) gate to bulk $\Rightarrow C_1 \parallel C_2$

3) $C_{oB}, C_{sB} \Rightarrow$ depends on bias voltage with substrate.

Case II :- when device is in triode, $V_{GS} < V_{Th}$ $V_S = V_D$

1) the gate to channel capacitance is divide between source & drain.

1) $C_{qD} = C_{qS} = C_{ov}W + \frac{C_{ox}WL}{2}$

 

Case III :- when device is in saturation.
 $V_{GS} < V_{Th}$ $V_{GS} - V_T < V_{DS}$.

$$C_{qS} = \frac{2}{3} C_{ox}WL + C_{ov}W$$

$$C_{qD} = C_{ov}W$$

* the capacitance doesn't provide smooth transition from one region to other. this will create difficult to converge in simulation.

* C_{qB} is neglected in saturation & triode region. because of formation of channel which act as a shield between gate & bulk.

Mos small signal model

→ Small signal analysis is applied when perturbation is small & non-linear effect are not concerned.

→ drain current is the function of drain voltage which is modelled by

$$\delta_o = \frac{\partial V_{os}}{\partial I_o} = \frac{1}{\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_{th})^2 \lambda} = \frac{1}{I_o \lambda}$$


→ the bulk potential effect the threshold voltage of mosfet. It effect the current I_o . it behave as the second gate.

$$g_{mb} = \frac{\partial I_o}{\partial V_{bs}} = \mu_n C_{ox} \frac{W}{L} (V_{gs} - V_T) \frac{\partial V_{Th}}{\partial V_{BS}}$$

$$\frac{\partial V_{Th}}{\partial V_{os}} = -\frac{\partial V_{Th}}{\partial V_{SB}} = -\frac{\gamma}{2} (2\phi_F + V_{SB})^{-1/2}$$

$$g_{mb} = g_m \eta \quad \text{where } \eta = -\frac{\gamma}{2} (2\phi_F + V_{SB})^{-1/2}$$

Small signal model.

 

→ For pmos the small signal is similar to that of nmos.

level one Spice parameters:-

- * V_{TO} :- threshold voltage with zero $V_{SB} \rightarrow V$
- * γ :- body-effect coefficient $\rightarrow V^{1/2}$.
- * ϕ :- $2\phi_F \rightarrow V$
- * t_{ox} :- gate oxide thickness $\rightarrow m$.
- * N_{sub} :- Substrate doping $\rightarrow cm^{-3}$
- * L_D :- source/drain side diffusion $\rightarrow m$.
- * μ_0 :- channel mobility $\rightarrow cm^2/V$.
- * λ :- channel-length modulation coefficient $\rightarrow V^{-1}$
- * C_{j0} :- source/drain bottom-plate junction capacitance per unit area $\rightarrow F/m^2$
- * C_{jsw} :- sidewall junction capacitance per unit length $\rightarrow F/m$.
- * ϕ_B :- source/drain junction built-in potential $\rightarrow V$
- * m_j :- exponent in C_{j0} equation \rightarrow unitless
- * m_{jsw} :- exponent in C_{jsw} equation \rightarrow unitless.
- * C_{gd0} :- gate-drain overlap capacitance per unit width $\rightarrow F/m$.
- * C_{gs0} :- gate-source overlap capacitance per unit width $\rightarrow F/m$.
- * J_s :- source/drain leakage current per unit area $\rightarrow A/m^2$


SINGLE STAGE AMPLIFIERS.

* The ideal input and output relation of amplifier $y(t) = a_0 + a_1 x(t)$.

* the real input & output relation of amplifier due to distortion is given by $y(t) = a_0 + a_1 x(t) + \underbrace{a_2 x^2(t) + a_3 x^3(t) + \dots}_{\text{higher order harmonics.}}$

* Parameters that used to evaluate the performance of amplifier are
1) speed 2) gain 3) maximum swing 4) power consumption
5) supply Voltage 6) linearity 7) input output impedance.


Amplifier categories

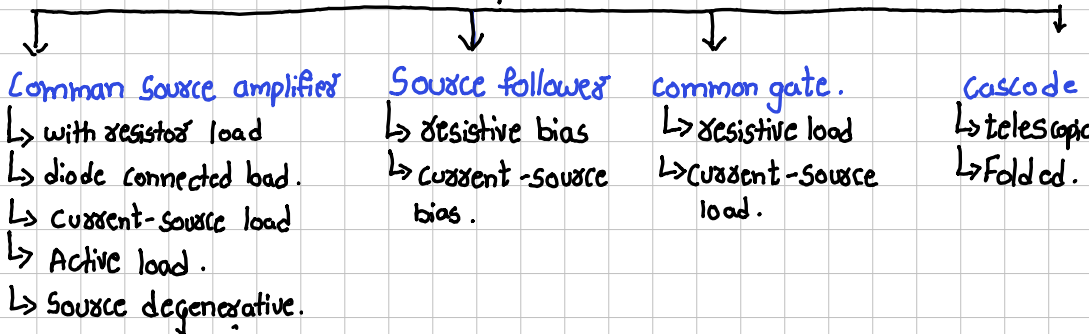

Common Source Stage. [CS].

* CS with Resistance.
 
$$\therefore V_{out} = V_{DD} - R_d \times \left[\frac{1}{2} C_{ox} W L u_n (V_{GS} - V_{TH})^2 \right]$$



triode region $V_{out} < V_{in} - V_{TH}$.

$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = -R_o u_n C_{ox} \frac{W}{L} (V_{in} - V_{TH}) = -g_m R_o. =$$

- * Since g_m is function of V_{in} the swing of signal should be small to prevent non linear behaviour.

$$A_v = - \sqrt{2 u_n C_{ox} \frac{W}{L} I_D} \frac{V_{DD}}{I_D} \Rightarrow - \sqrt{2 u_n C_{ox} \frac{W}{L}} \frac{V_{DD}}{\sqrt{I_D}}$$

- * A_v can be increased by increasing W/L which in lead to increase in cap & high V_{DD} which will reduce the swing
- * if V_{DD} is kept constant and I_D is reduced which will increase R_o & the time constant
- * for large R_o the channel length modulation become significant.


$$\frac{\partial V_{out}}{\partial V_{in}} = -R_o C_{ox} \frac{W}{L} u_n (V_{in} - V_{TH}) (1 + \lambda V_{DS}) - \frac{R_o C_{ox} \frac{W}{L}}{2} (V_{in} - V_{TH})^2 \lambda \frac{\partial V_{out}}{\partial V_{in}}$$

$$A_v = -g_m R_o \frac{-R_o}{\delta_o} A_v = A_v = -g_m [R_o \parallel \delta_o].$$

- * gain is achieved when $R_o = \infty$ ie $= -g_m \delta_o$ which is almost equal to 10.

CS stage with diode connected load.

 It is difficult to fabricate resistor on chip so we use diode connected resistor to get resistor. the resistance of diode connected resistor is equal to.



$$\delta = \frac{1}{g_{mp} + g_{mbp}} \parallel \delta_{op} \approx \frac{1}{g_{mp} + g_{mbp}}.$$

$$\therefore \text{gain } A_v = -g_{mn} \delta \parallel \delta_{on} = \frac{-g_{mn}}{g_{mp} + g_{mbp}} \parallel \delta_{on} \approx \frac{-g_{mn}}{g_{mp} + g_{mbp}}.$$

$$\therefore A_v = \frac{-g_{mn}}{g_{mp}(1 + \eta)} = \frac{\sqrt{\frac{W}{L} \times u_n}}{\sqrt{\frac{W}{L} \times u_p}} \times \frac{1}{(1 + \eta)} \quad \eta = \frac{g_{mbp}}{g_{mp}}$$

* the gain is independent of bias current or voltage it is more linear compared to previous amplifiers.


* gain is weak function of W/L if $u_n = 2u_p$ then $(W/L)_n = 12.5(W/L)_p$ to get gain of 5.

* In today technology channel length modulation can't be ignored \therefore gain is given by

$$A_v = \frac{-g_{mn}}{g_{mp} + g_{mbp}} \parallel \delta_{o1} \parallel \delta_{o2}.$$

CS Stage with current source.

 - * to achieve higher gain we need to have larger R_o in order to achieve that we use current source.



$$A_v = -g_m (\delta_{o1} \parallel \delta_{o2})$$

- to achieve larger swing V_{dsat} of M_2 should be less. this can be achieved by increasing width, but this will lead to reduction of δ_{o2} . then we have to change λ by increasing length to increase δ_{o2} . but increasing in width will also increase the capacitance at output node.


$$g_{m1} \delta_{o1} = \sqrt{2 \left(\frac{W}{L} \right) \mu_n C_{ox} I_0} \frac{1}{I_0 \lambda}$$

- * gain increase. with increasing L as λ is function of L .
- * gain increase with decrease in I_0
- * increase in length of M_2 will increase δ_{o2} but it will also increase the V_{dsat} of M_2 .

CS Stage with active load

- * the gain of the following circuit is
 
$$A_v = -(g_{m1} + g_{m2}) (\delta_{o1} \parallel \delta_{o2})$$




- * the following circuit has same impedance as current source circuit but it has higher gain compared to current source.
- * Since $V_{GS1} + |V_{GS2}| = V_{DD}$. the variation in V_{DD} or V_{TH} will translate.

to current at output. the bias point of the circuit depends upon the PVT. this is the drawback of the circuit.

* the output gain given by variation in supply

$$V_{out} = (g_{m2} V_{DD} \delta o_2 + V_{DD}) \frac{\delta d o_r}{\delta d o_2 + \delta d o_1}$$

 
$$\therefore \frac{V_{out}}{V_{DD}} = \frac{(g_{m2} \delta o_2 + 1) \delta d o_r}{\delta d o_2 + \delta d o_1}$$



- CS with triode load.

* here mosfet is operating in deep triode.
 
$$R_{on} = \frac{1}{\frac{W_2}{L_2} \mu_{n2} U_{T2} (V_{DD} - V_b - U_T)}$$



* the drawback of the following circuit is the R_{on} depend on V_b, V_T, W, L, V_{DD} which change with PVT. and it is difficult to produce constant bias voltage V_b .

CS with source degenerated.

* this configuration will make output more linear compared to other configuration. it make gain less dependent on g_m

* the output of this circuit is linearized but the gain is reduced due to the feed back.

$$G_m = \frac{\partial I_o}{\partial V_{in}} = \frac{\partial I_o}{\partial V_{GS}} \times \frac{\partial V_{GS}}{\partial V_{in}} \quad (1)$$

We know that

$$V_{GS} = V_{in} - I_o R_s$$

$$\therefore \frac{\partial V_{GS}}{\partial V_{in}} = \left(1 - \frac{\partial I_o}{\partial V_{in}}\right) R_s \Rightarrow (1 - G_m) R_s \quad (2)$$

Substitute 2 in (1).

$$G_m = g_m (1 - G_m) R_s \Rightarrow G_m = \frac{g_m}{1 + g_m R_s}$$

$$\therefore \text{Small signal gain} = -G_m R_o = \frac{-g_m R_o}{1 + g_m R_s} \approx \frac{-R_o}{R_s} \text{ if } g_m R_s \gg 1.$$

* Gain of source degenerative circuit with body effect and channel length modulation is given below.



$$\therefore I_{out} = g_m V_i - g_{mb} V_x - \frac{I_{out} R_s}{\delta_o}$$

$$I_{out} = g_m (V_{in} - I_{out} R_s) + g_{mb} (-I_{out} R_s) - \frac{I_{out} R_s}{\delta_o}$$

$$G_m = \frac{g_m \delta_o}{R_s + [1 + (g_m + g_{mb}) R_s] \delta_o}$$


$$A_v = \frac{-g_m \delta_o \parallel R_{eq}}{R_s + [1 + (g_m + g_{mb}) R_s] \delta_o}$$
  
$$R_{eq} = R_o \parallel [R_s + \delta_o + (g_m + g_{mb}) \delta_o R_s]$$



finding gain by inspection for source degeneration

 gain is equal to impedance looking into drain.
divide by the impedance looking into the source $\Rightarrow c$.




$$A_v = \frac{-R_D}{\frac{1}{g_m} + R_D} \Rightarrow \frac{R_{AB}}{R_{BC}} = \frac{-R_D}{\frac{1}{g_m} + R_S}$$

* after source degeneration output resistance is increase therefore output resistance is


$$R_{out} = \left[1 + (g_m + g_{mb}) R_S \right] r_o + R_S \parallel R_D$$

 * any circuit can be represented by noxtan equivalent circuit.
by short circuit current parallel with open circuit resistance.
and gain is given by $-g_m R_{eq}$.



Source follower \rightarrow Common drain.

 
* To achieve large gain for common source we need to have large output resistance. When this is connected to next stage with low impedance, the effective impedance decreases, so the voltage gain. We can use source follower as a buffer between two stages. The gain of source follower is almost equal to 1.



$$V_{gs} = -V_{out}$$

$$V_{out} = R_s [g_m V_i - g_{mb} V_{out}]$$
 
$$V_{out} = R_s [g_m [V_{in} - R_s V_{out}] - g_{mb} V_{out}]$$



$$\frac{V_{out}}{V_{in}} = \frac{g_m R_s}{1 + [g_m + g_{mb}] R_s} \quad \text{if } (g_m + g_{mb}) R_s \gg 1 \approx \frac{g_m}{g_m + g_{mb}} \approx \frac{1}{1 + \eta} =$$

- * Even $R_s = \infty$ the output gain will not be equal to 1.
- * If V_{in} increases by $\sqrt{2}$, I_{out} & V_{out} will increase by 2. This will create non-linearity in gain. To resolve this issue, output resistance is replaced by a constant current source.

* It has high input impedance & moderate output impedance.

* It has low output headroom for swing.

Common gate.

$$* V_{out} = V_{DD} - \frac{1}{2} \mu_0 C_{ox} \frac{W}{L} (V_b - V_{in} - V_{Th})^2 R_D.$$

\therefore



$$\frac{\partial V_{out}}{\partial V_{in}} = -\frac{1}{2} \mu_0 C_{ox} \frac{W}{L} (V_b - V_{in} - V_{Th}) \left(-1 - \frac{\partial V_{Th}}{\partial V_{in}} \right) R_D.$$

$$\frac{\partial V_{Th}}{\partial V_{in}} = \frac{\partial V_{Th}}{\partial V_{SB}} \frac{\partial V_{SB}}{\partial V_{in}} = \eta \times \frac{\partial V_{in}}{\partial V_{in}} = \eta$$

$$A_v = +\frac{1}{2} \mu_0 C_{ox} \frac{W}{L} (V_b - V_{in} - V_{Th}) (1 + \eta) R_D.$$

$$A_v = g_m (1 + \eta) R_D.$$
  
$$\text{gain by inspection} = \frac{\text{Impedence at drain } (R_D) - R_D}{\text{Impedence at source } (R_D) \times (g_m + g_{mb})} = (g_m + g_{mb}) R_D$$




* gain considering δ_o & R_S .

$$V_i = +\frac{R_S V_{out}}{R_D} - V_{in}. \quad (1)$$

$$\delta_o \left[\frac{-V_{out}}{R_D} - g_m V_i - g_{mb} V_i \right] - \frac{V_{out} R_S + V_{in}}{R_D} = V_{out} \quad (2)$$


from 1 & 2.
 
$$A_v = \frac{(g_m + g_{mb}) \delta_o + 1}{\delta_o + (g_m + g_{mb}) \delta_o R_S + R_S + R_D} R_D$$




* Input impedance at the source is
 
$$R_{in} = \frac{R_D + r_o}{1 + (g_m + g_{mb})r_o}$$



Cascode stage.

 * the input from common source is converted into current & this current is feed to common gate this type of configuration is called cascode stage



* M_1 provide the gain to small signal V_{in} & M_2 route the current to the R_D . device M_1 is called input device & device M_2 is called cascode. the device configuration is called telescopic cascode.

* let us consider if we apply ΔV voltage to V_{in} . and $r_o = \lambda = 0$. $r_{o2} = \infty$ then output current is $g_{m1}\Delta V$. the voltage at V_x is $(1/g_{m2})g_{m1}\Delta V$ & the voltage at the output is $R_D g_{m1}\Delta V$.


* let us consider if we keep V_{in} constant & vary V_b . the Mosfet M_1 act as a current source. the node X act as source follower which has gain equal to 1. the node output doesn't change with the input due to constant current is flowing in the circuit.

* To get both the device into saturation we need to have $V_{out} \geq V_{dsat1} + V_{dsat2}$.

$$A_v = -I_D R_D$$

$$I_D = \frac{R_p}{R_p + \frac{1}{g_{m1} + g_{m2}}} g_{m1} V_{in}$$

 
current divider between resistance at M_2 & R_p .



$$A_v = \frac{-R_p}{R_p + \frac{1}{g_{m1} + g_{m2}}} g_{m1} V_{in}$$

$$R_{in} \text{ of figure 2} = \delta o_2 + \delta o_1 + (g_{m2} + g_{mb}) \delta o_2 \delta o_1$$
 
$$\approx (g_{m2} + g_{mb}) \delta o_2 \delta o_1$$




gain for figure 3 is

$$A_v = G_m R_{out}$$

$$R_{out} = \delta o_1 + \delta o_2 + (g_{m2} + g_{mb2}) \delta o_2 \delta o_1$$
 
$$I_{out} = \frac{\delta o_2 g_{m1} V_{in}}{\delta o_2 + \left(\frac{1}{g_{m1} + g_{mb2}} \right) \parallel \delta o_2}$$




$$A_v = G_m R_{out} \Rightarrow g_{m1} \delta o_1 \left[(g_{m2} + g_{mb2}) \delta o_2 + 1 \right]$$

The output impedance of figure 1 is .

$$\left[\delta_{o4} + \delta_{o3} + (g_{m3} + g_{m_{b3}}) \delta_{o3} \delta_{o4} \right] \parallel \left[\delta_{o2} + \delta_{o1} + (g_{m2} + g_{m_{b2}}) \delta_{o1} \delta_{o2} \right]$$

 
$$\text{gain } A_v \approx .g_{m1} \left[(g_{m3} + g_{m_{b3}}) \delta_{o3} \delta_{o4} \parallel (g_{m2} + g_{m_{b2}}) \delta_{o1} \delta_{o2} \right]$$



* Since cascode has high impedance it can be used as shield for voltage variations. in the circuit.

Folded Cascode.

 
* Cascode circuit can also be made by using PMOS - NMOS or NMOS - PMOS configuration.



* the current $I_x = I_1 + I_2$

* In fig 2 V_{in} become more positive. I_1 decrease. forcing I_{o2} to increase. hence V_{out} to drop.

 * if V_{in} (figure 2) decrease from V_{DD} to zero M_2 carries all current & $V_{in} < V_{DD} - V_{th}$. then $I_2 = I_x - I_1$, $V_{out} = V_{DD} - I_2 R_D$.



* if V_{in} is decreased further. $I_1 = I_x$ & $I_2 = 0$.

* if V_{in} falls below this level ie $I_1 > I_x$ then M_1 enters into triode region.

